

date: 27 may 2020

course: Logic design

Topic: 1. Boolean equation &  
conversion of Mux and  
decoder to logic gates

2. 7 segment decoder

github repository: Shradha-courses

Name: SHRADHA

USN: HALITECO88

Semester &

Section: 4th sem

'A' section

Boolean algebra:

"In 1854, George Boole developed an algebraic system now called Boolean algebra"

\* "Boolean algebra is a system of mathematical logic"

\* "It is defined with set of elements, a set of operators, and a number of axioms or postulates"

Axioms and laws of Boolean algebra:

Axioms or postulates of Boolean algebra are a logical expressions upon which we can build useful theorems

"AND operation" "OR operation" "NOT operation"


MUX to logic gates:

- ① NAND, NOR - universal gates.
- ② "Universal logic"
- ③ MUX and decoder are called "Universal logic"

what is multiplexer?

- multiplexer is a device that selects one of several analog or digital input signals and it forward it to output line that is signal output line here the general equation of MUX is  $2^n - 1$

2:1 MUX

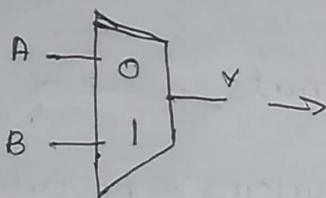

selection(s)	output(Y)
0	A
1	B

with the help of KMAP  $\Rightarrow Y = A\bar{S} + BS$

date: 26 may

course: python

Topic: ~~application~~

① application: build  
a desktop database  
application

Name: SHRADHA

USN: HALITECO88

Semester: 1E

section: 4th sem

'A' sec

Build a desktop database Application

- \* how the output will look like
- \* Use interface design
- \* connecting the frontend to the Backend
- \* fixing the bug
- \* Creating a standalone Executable version of the program